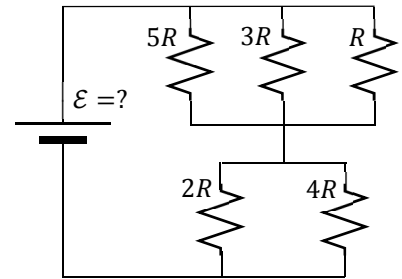


27.11½ Consider the circuit at right. Assume all resistances are known but potential difference across the battery is unknown. A student uses an ammeter in the lab and discovers current through resistor $2R$ is I .

- Determine equivalent resistance of the circuit.
- Determine potential difference across the battery.



27.11 $\frac{3}{4}$ In the circuit at right, all resistances are R with the exception of the one in the figure marked r . Assume R is known but r is unknown. Potential difference \mathcal{E} across the battery is known. Furthermore, a student discovers power delivered by the battery changes by 5.55% when the switch is closed.

- Does total resistance *increase* or *decrease* when the switch is closed?
- Does power delivered by the battery *increase* or *decrease* by 5.55%?
- Determine the resistance r as decimal number with 3 sig figs times R .

